
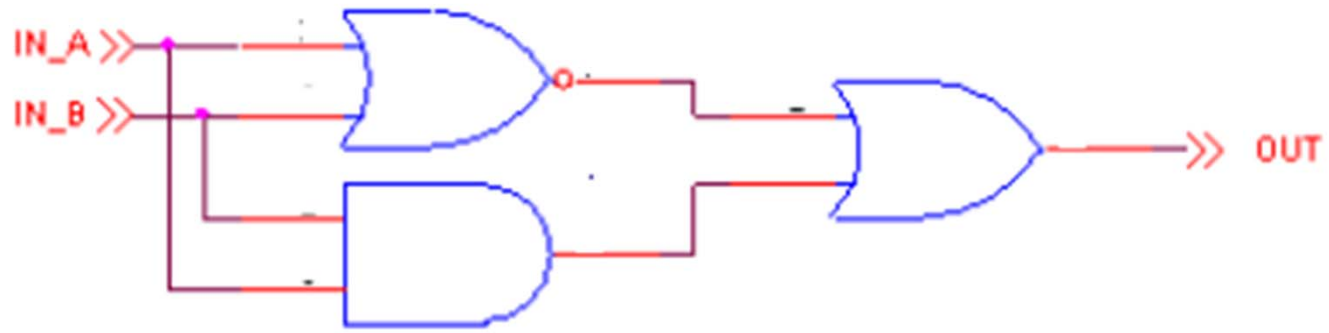


# Exercício Circuitos


1)

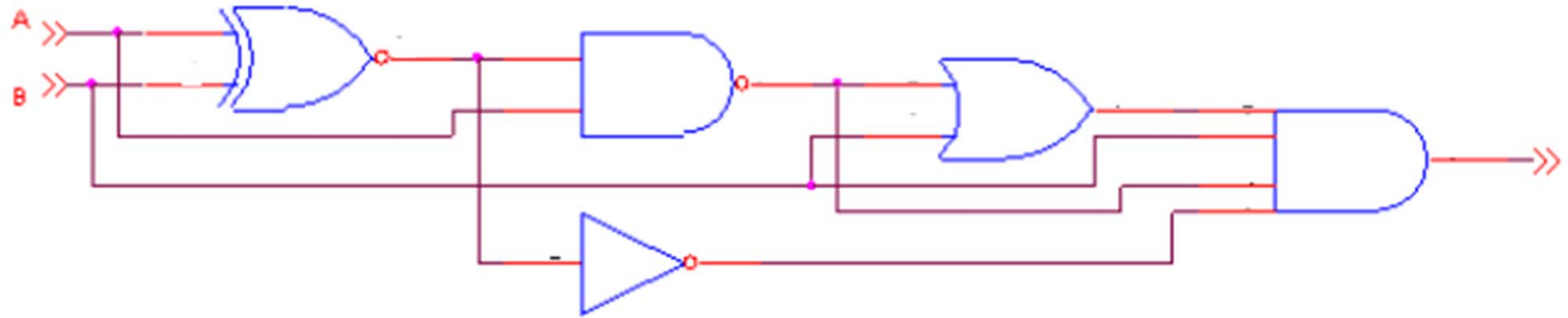

2)




3)

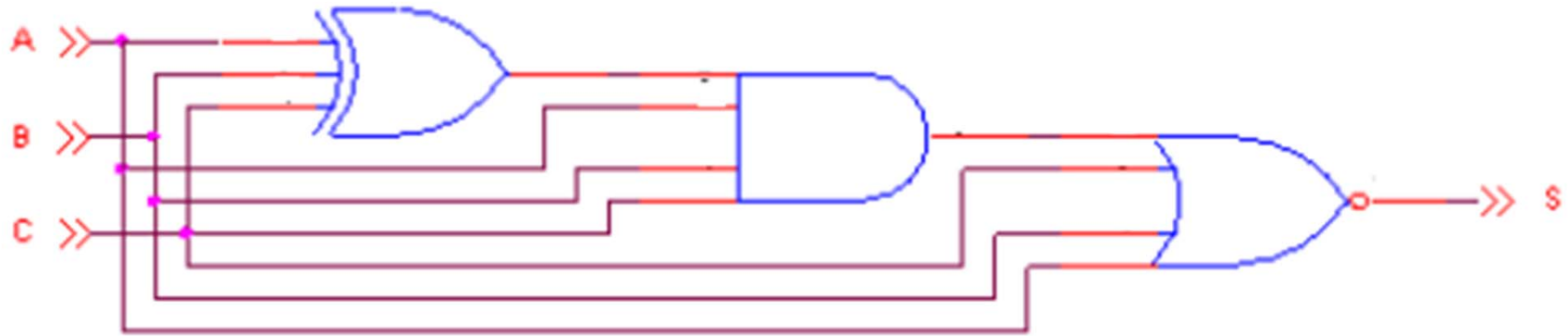

A = 1 ; B = 0 ; C = 1

4)

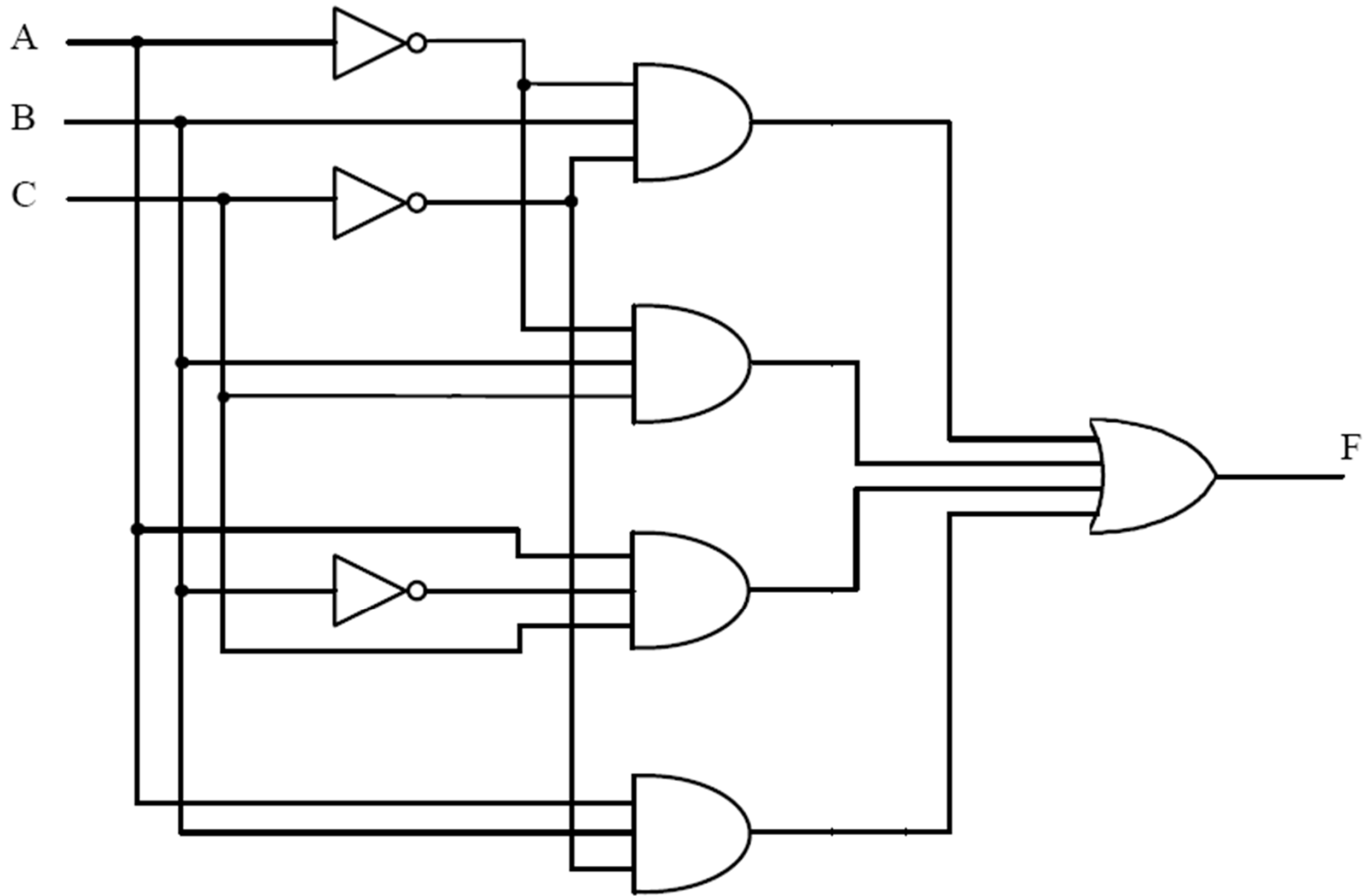

$A = 0 ; B = 1 ; C = 0$